

SR flip-flop

S(t)	R(t)	Q(t+1)	Operation
0	0	Q(t)	No Change
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined

Characteristic Table

$$Q(t+1) = S(t) + R'(t)Q(t)$$

Characteristic equation

JK flip-flop

J(t)	K(t)	Q(t+1)	Operation
0	0	Q(t)	No Change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Characteristic Table

$$Q(t+1) = J(t)Q'(t) + K'(t)Q(t)$$

Characteristic equation

D flip-flop

D(t)	Q(t+1)	Operation
0	0	Reset
1	1	Set


Characteristic Table

$$Q(t+1) = D(t)$$

Characteristic equation

$$T_A = Y \quad , \quad T_B = \bar{X}.A.Y$$

Present State		Inputs							Next State		Output
A(t)	B(t)	X	Y	\bar{X}	\bar{B}	T_A	T_B	A	A(t+1)	B(t+1)	Z
0	0	0	0	1	1	0	0	0	0	0	1
0	0	0	1	1	0	1	1	1	1	1	0
0	0	1	0	0	1	0	0	0	0	0	0
0	0	1	1	0	1	1	0	1	1	0	0
0	1	0	0	1	1	0	0	0	0	0	1
0	1	0	1	1	0	1	1	1	1	1	0
0	1	1	0	0	1	0	0	0	0	0	0
0	1	1	1	0	1	1	0	1	1	0	0
1	0	0	0	1	1	0	0	0	0	0	1
1	0	0	1	1	0	1	1	1	1	1	0
1	0	1	0	0	1	0	0	0	0	0	0
1	0	1	1	0	1	1	0	1	1	0	0
1	1	0	0	1	1	0	0	0	0	0	1
1	1	0	1	1	0	1	1	1	1	1	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	1	1	0	1	1	0	0

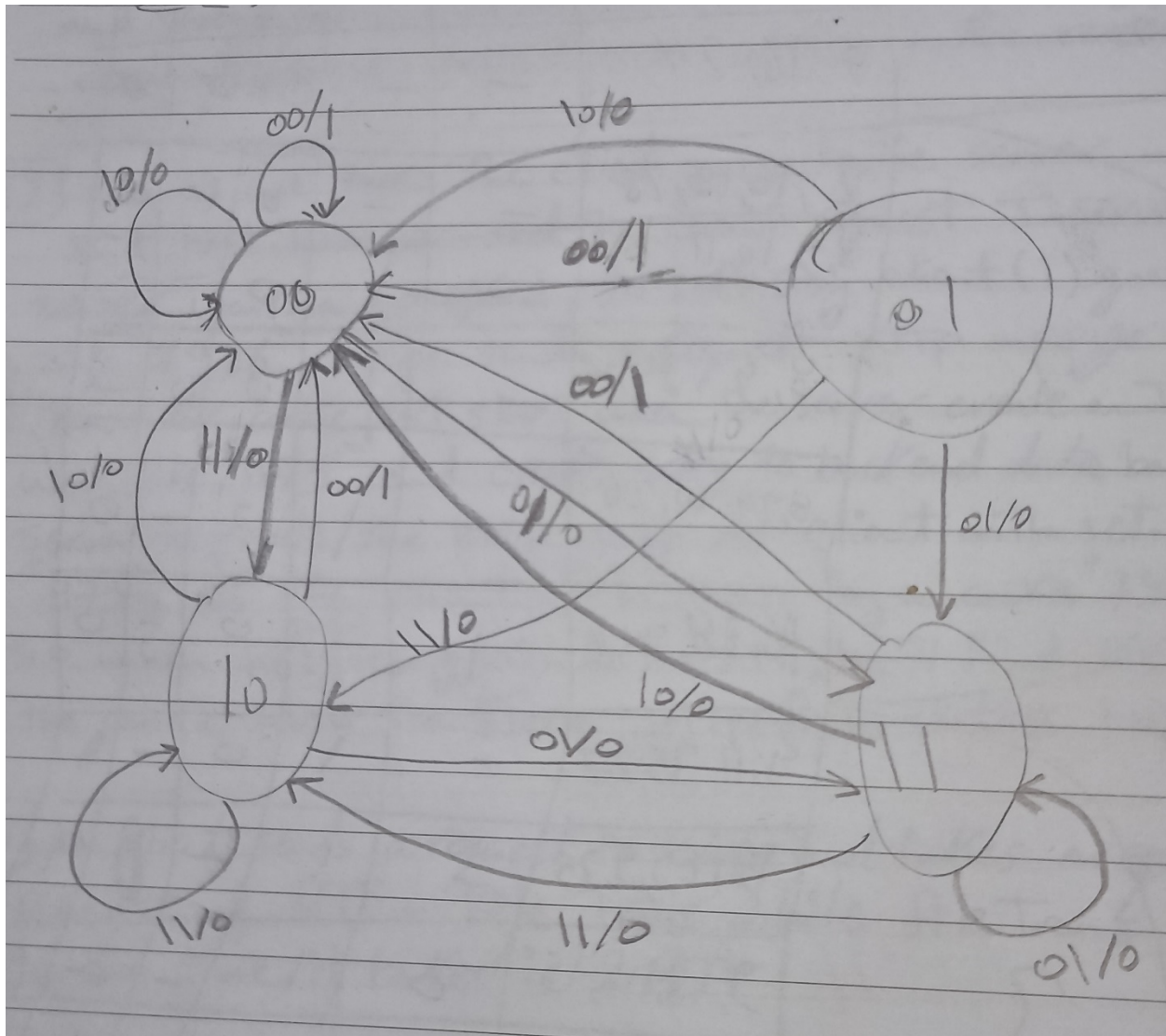

3.d

Present state	Input X	Next state	Output Z
00	0	00	0
00	1	01	1
01	0	11	0
01	1	01	0
10	0	10	0
10	1	11	1
11	0	01	0
11	1	10	0

SR flip-flop

Present State		Input						Next State		Output
A(t)	B(t)	X	\bar{B}	S_A	R_A	S_B	R_B	A(t+1)	B(t+1)	Z
0	0	0	1	0	X	0	X	0	0	0
0	0	1	1	0	X	1	0	0	1	1
0	1	0	0	1	0	X	0	1	1	0
0	1	1	0	0	X	X	0	0	1	0
1	0	0	1	X	0	0	X	1	0	0
1	0	1	1	X	0	1	0	1	1	1
1	1	0	0	0	1	0	X	0	1	0
1	1	1	0	X	0	X	1	1	0	0

A	BX	00	01	11	10
	0	0	0	0	1
1	X	X	X	X	0

S_t	R_t	Q(t)	Q(t+1)
0	X	0	0
0	1	X	0
1	0	X	1
X	1	X	0

State equations

$S_A = \bar{A}.B.\bar{X}$

$R_A = A.B.\bar{X}$

$S_B = X$

$R_B = A.B$


$Z = \bar{B}.X$


A	BX	00	01	11	10
	0	X	X	X	0
1	0	0	0	0	1

A	BX	00	01	11	10
	0	0	1	X	X
1	0	1	X	0	

A	BX	00	01	11	10
	0	X	0	0	0
1	X	0	1	X	

BX \ A	00	01	11	10
0	0	1	0	0
1	0	1	0	0

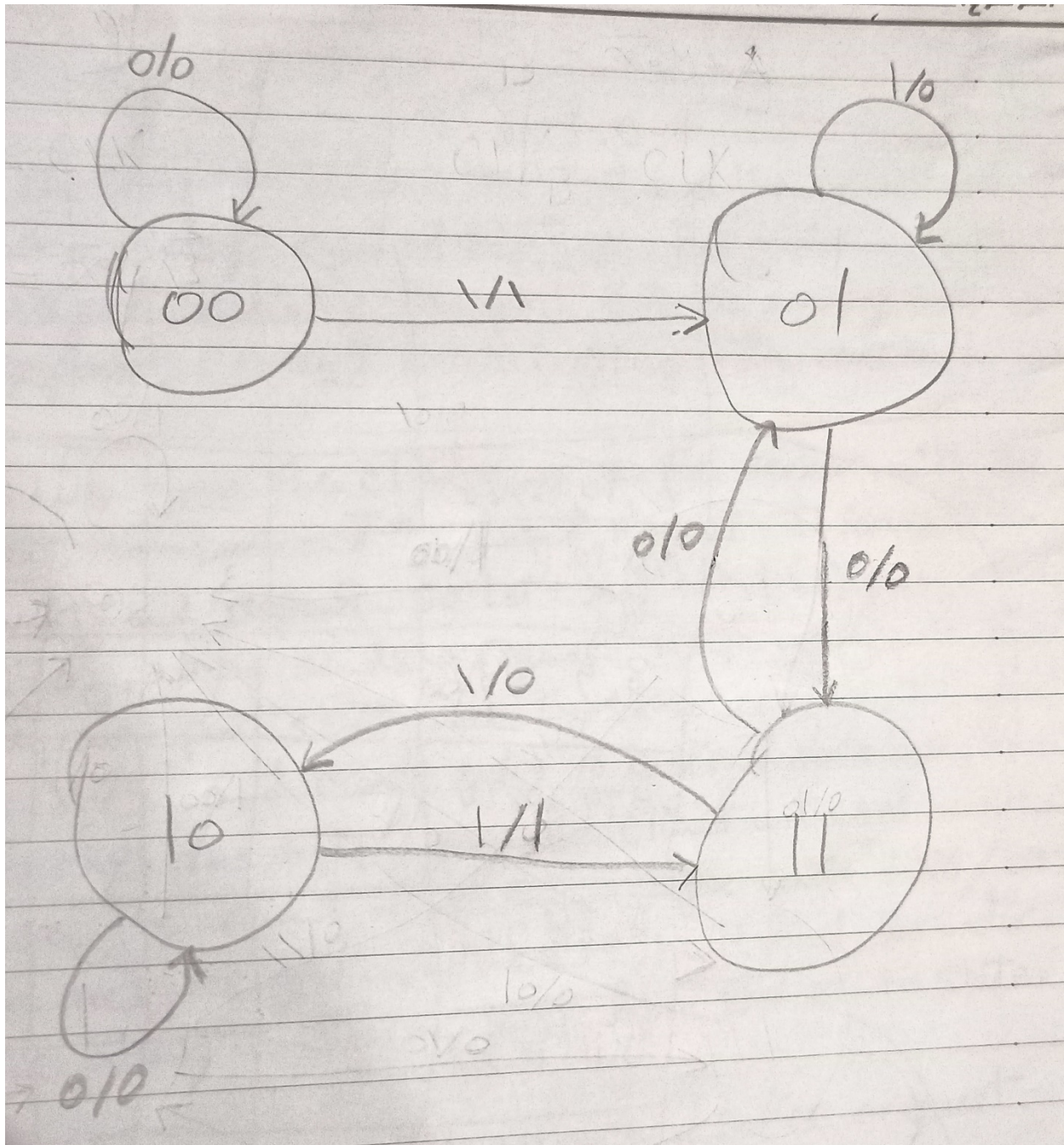

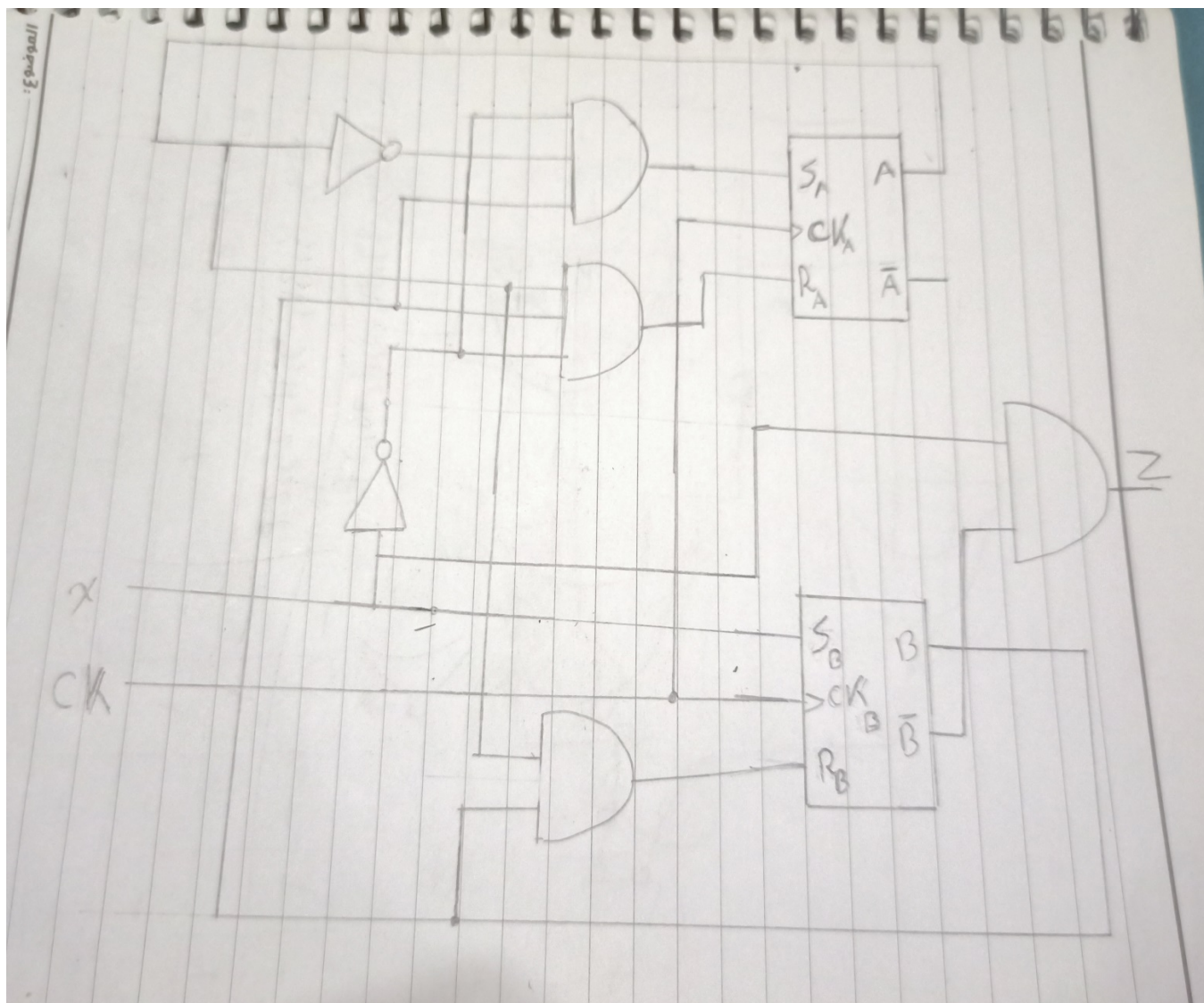

JK flip-flop

Present State		Input						Next State		Output
A(t)	B(t)	X	\bar{B}	J_A	K_A	J_B	K_B	A(t+1)	B(t+1)	Z
0	0	0	1	0	X	0	X	0	0	0
0	0	1	1	0	X	1	0	0	1	1
0	1	0	0	1	0	X	0	1	1	0
0	1	1	0	0	X	X	0	0	1	0
1	0	0	1	X	0	0	X	1	0	0
1	0	1	1	X	0	1	0	1	1	1
1	1	0	0	X	1	X	0	0	1	0
1	1	1	0	X	0	X	1	1	0	0

		BX	00	01	11	10
A	0		0	0	0	1
	1		X	X	X	X

State equations

$$J_A = B.\bar{X}$$

$$K_A = A.B.\bar{X}$$

$$J_B = X$$

$$K_B = A.B.X$$

$$Z = \bar{B}.X$$

		BX	00	01	11	10
A	0		X	X	X	0
	1		0	0	0	1

		BX	00	01	11	10
A	0		0	1	X	X
	1		0	1	X	X

		BX	00	01	11	10
A	0		X	0	0	0
	1		X	0	1	0

BX \ A	00	01	11	10
0	0	1	0	0
1	0	1	0	0

